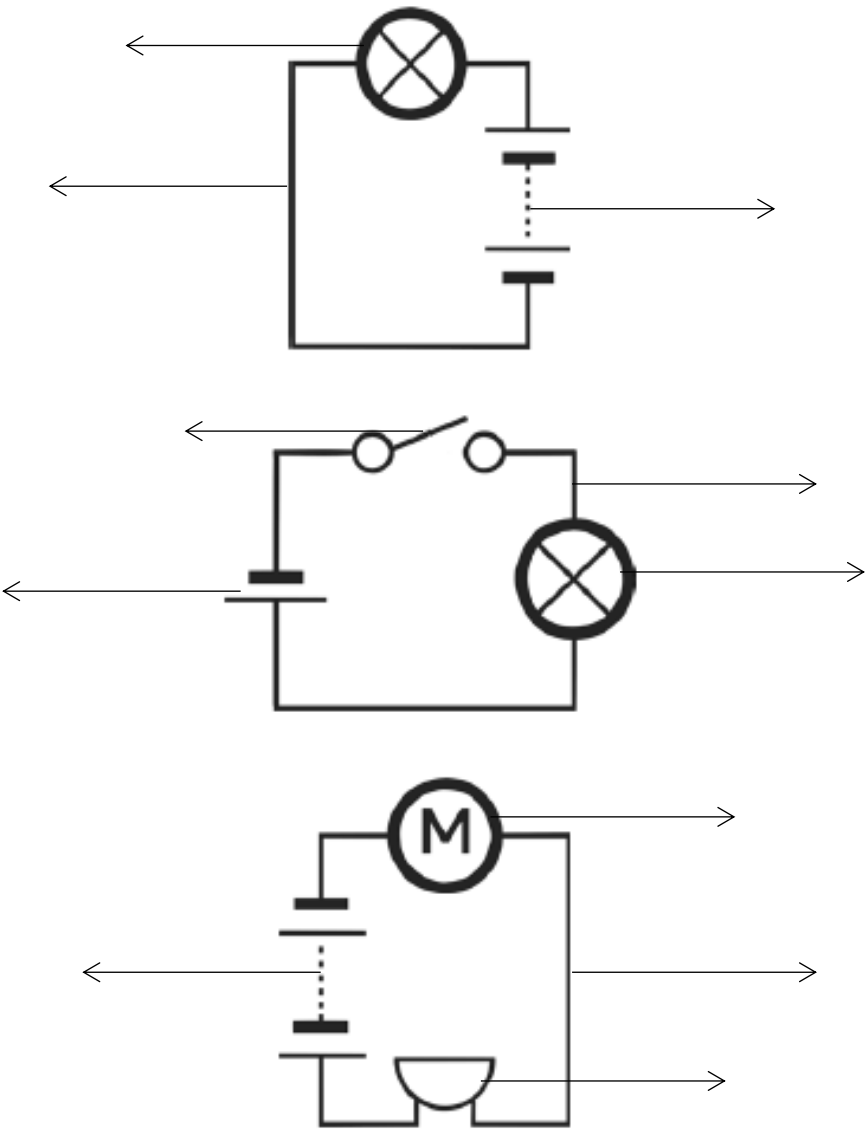


Look at the circuit diagrams and label each component: (use the internet to help you)



Draw the following circuit using the scientific circuit symbols.

1. Circuit should contain: a bulb, a cell and an open switch	
2. Circuit should contain: a battery and two motors	
3. Circuit should contain: a buzzer, a battery and a closed switch	